

邏輯設計 Hw#5

Answer

1. Design a combinational circuit that forms the 2-bit binary sum S_1S_0 of two 2-bit number A_1A_0 and B_1B_0 and has both a carry input C_0 and carry output C_2 . Design the entire circuit implementing each of the three outputs with a two-level circuit plus inverters for the input variables. Begin the design with the following equations for each of the two bits of the adder:

$$S_i = A_i'B_i'C_i + A_i'B_iC_i' + A_iB_i'C_i' + A_iB_iC_i$$

$$C_{i+1} = A_iB_i + A_iC_i + B_iC_i$$

<Ans>

就是把要求的outputs, S_1, S_0, C_2 down 到用inputs A_1, A_0, B_1, B_0, C_0 表示

$$C_1 = A_0B_0 + A_0C_0 + B_0C_0$$

$$S_0 = A_0'B_0'C_0 + A_0'B_0C_0' + A_0B_0'C_0' + A_0B_0C_0$$

$$S_1 = A_1'B_1'C_1 + A_1'B_1C_1' + A_1B_1'C_1' + A_1B_1C_1$$

$$= A_1'B_1'(A_0B_0 + A_0C_0 + B_0C_0) + A_1'B_1(A_0B_0 + A_0C_0 + B_0C_0)' + A_1B_1'(A_0B_0 + A_0C_0 + B_0C_0)' + A_1B_1(A_0B_0 + A_0C_0 + B_0C_0)$$

$$= A_1'B_1'A_0B_0 + A_1'B_1'A_0C_0 + A_1'B_1'B_0C_0 + A_1'B_1A_0'B_0' + A_1'B_1A_0'C_0' + A_1'B_1B_0'C_0' + A_1B_1'A_0'B_0' + A_1B_1'A_0'C_0' + A_1B_1'B_0'C_0' + A_1B_1A_0B_0 + A_1B_1A_0C_0 + A_1B_1B_0C_0$$

$$C_2 = A_1B_1 + A_1C_1 + B_1C_1$$

$$= A_1B_1 + A_1(A_0B_0 + A_0C_0 + B_0C_0) + B_1(A_0B_0 + A_0C_0 + B_0C_0)$$

$$= A_1B_1 + A_1A_0B_0 + A_1A_0C_0 + A_1B_0C_0 + B_1A_0B_0 + B_1A_0C_0 + B_1B_0C_0$$

2. The following binary numbers have a sign in the leftmost position and, if negative, are in 2's complement form. Perform the indicated arithmetic operations and verify the answers.

(a) $100111 + 111001$

(b) $110001 - 010010$

Indicate if overflow occurs for each computation.

<Ans>

(a)

$$\begin{array}{r}
 111111 \\
 100111 \quad (-25) \\
 +111001 \quad +(-7) \\
 \hline
 1100000 \quad (-32) \\
 \Rightarrow 100000 \quad (-32) \text{ verified}
 \end{array}$$

\therefore MSB的carry in = carry out

\therefore 無overflow

(b) $- 010010 = + 101110$

$$\begin{array}{r}
 10 \\
 110001 \quad (-15) \\
 +101110 \quad +(-18) \\
 \hline
 1011111 \quad -33 \\
 \Rightarrow 011111 \quad +31 \text{ verified}
 \end{array}$$

\therefore MSB的carry in \neq carry out

\therefore overflow發生，所以兩個負數相加竟得到正數

3. Use contraction beginning with an 8-bit adder-subtractor **without carry out** to design an 8-bit circuit without carry out that increments its input by 00000010 for input $S = 0$ and decrements its input by 00000010 for input $S = 1$. Perform the design by designing the distinct 1-bit cells needed and indicating the type of cell use in each of the eight bit positions.

<Ans>

當 $S = 0$ ，就是加 00000010；當 $S = 1$ ，是減 00000010，也就是加 11111110
把 00000010、11111110 當作 $B_7 \sim B_0$ 。

$$B_0 = 0, C_0 = 0 \Rightarrow S_0 = A_0 \oplus 0 \oplus 0 = A_0$$


$$\Rightarrow C_1 = A_0 B_0 + A_0 C_0 + B_0 C_0 = 0$$

$$B_1 = 1, C_1 = 0 \Rightarrow S_1 = A_1 \oplus 1 \oplus 0 = A_1'$$

$$\Rightarrow C_2 = A_1 B_1 + A_1 C_1 + B_1 C_1 = A_1$$

(接下來就沒法化簡了，因為 $B_2 \sim B_7$ 可能是 0 也可能是 1)

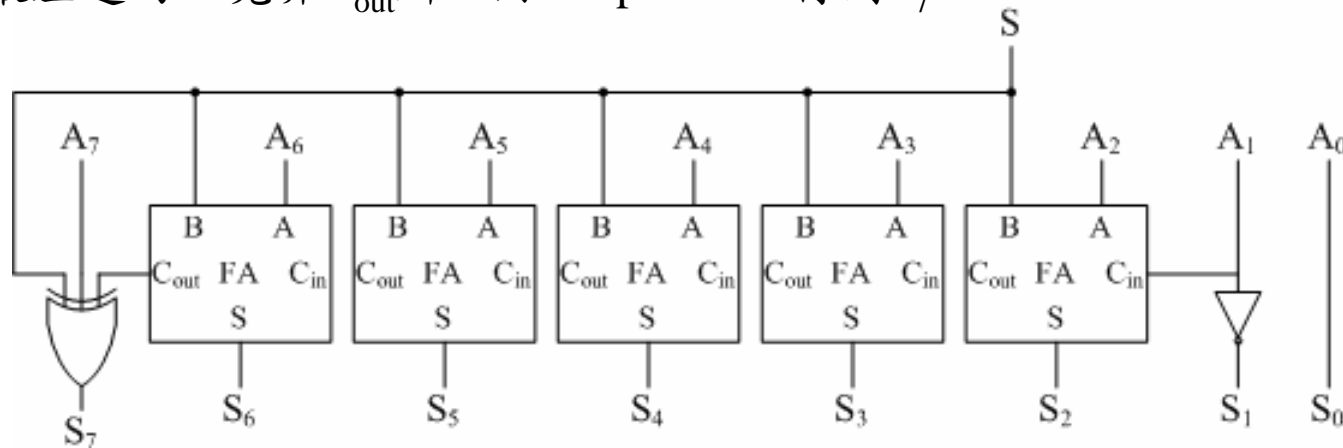S_0 直接拉線， S_1 接個 inverter， $S_{2 \sim 6}$ 是用 Full Adders 產生，
而最左邊的 bit 免算 C_{out} 所以用 3-input XOR 得到 S_7 。




4. Design a combinational circuit that compares two 4-bit unsigned numbers A and B to see whether B is greater than A. The circuit has one output X, so that $X = 1$ if $A < B$ and $X = 0$ if $A \geq B$.

<Ans>

$A < B$ ，發生在某一位置 $A_i = 0, B_i = 1$ ，而更高位都相等 ($A_j = B_j$, for all $j > i$)

$$\therefore X = A_3'B_3 + (A_3B_3 + A_3'B_3')A_2'B_2 + (A_3B_3 + A_3'B_3')(A_2B_2 + A_2'B_2')A_1'B_1 + (A_3B_3 + A_3'B_3')(A_2B_2 + A_2'B_2')(A_1B_1 + A_1'B_1')A_0'B_0$$


不經簡化的電路圖如下(不畫沒關係)：

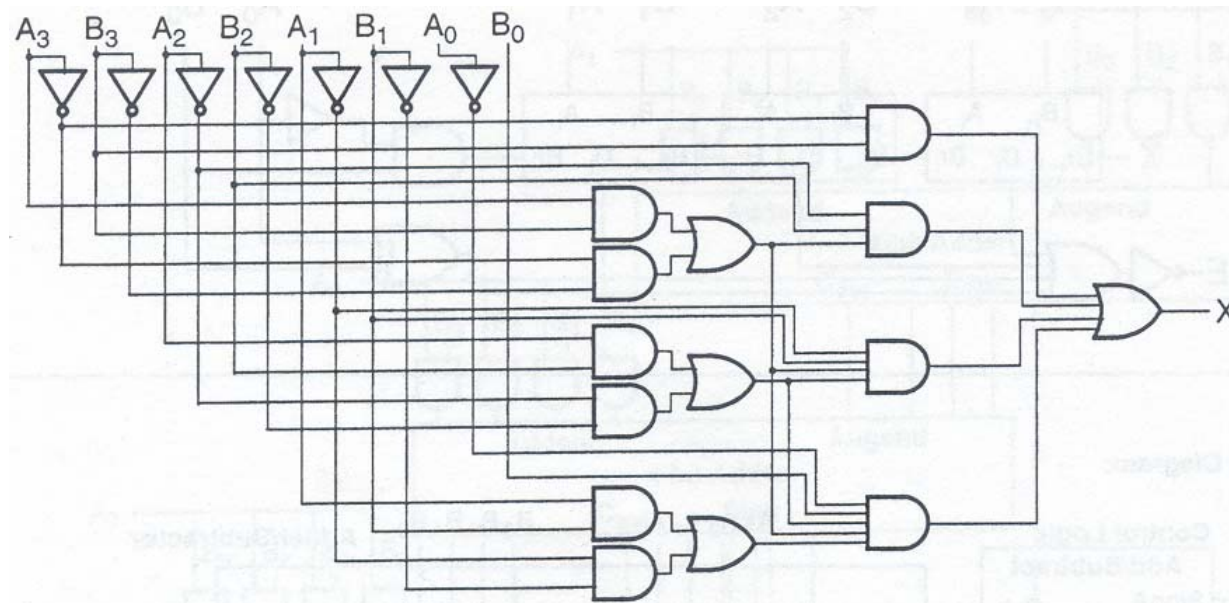

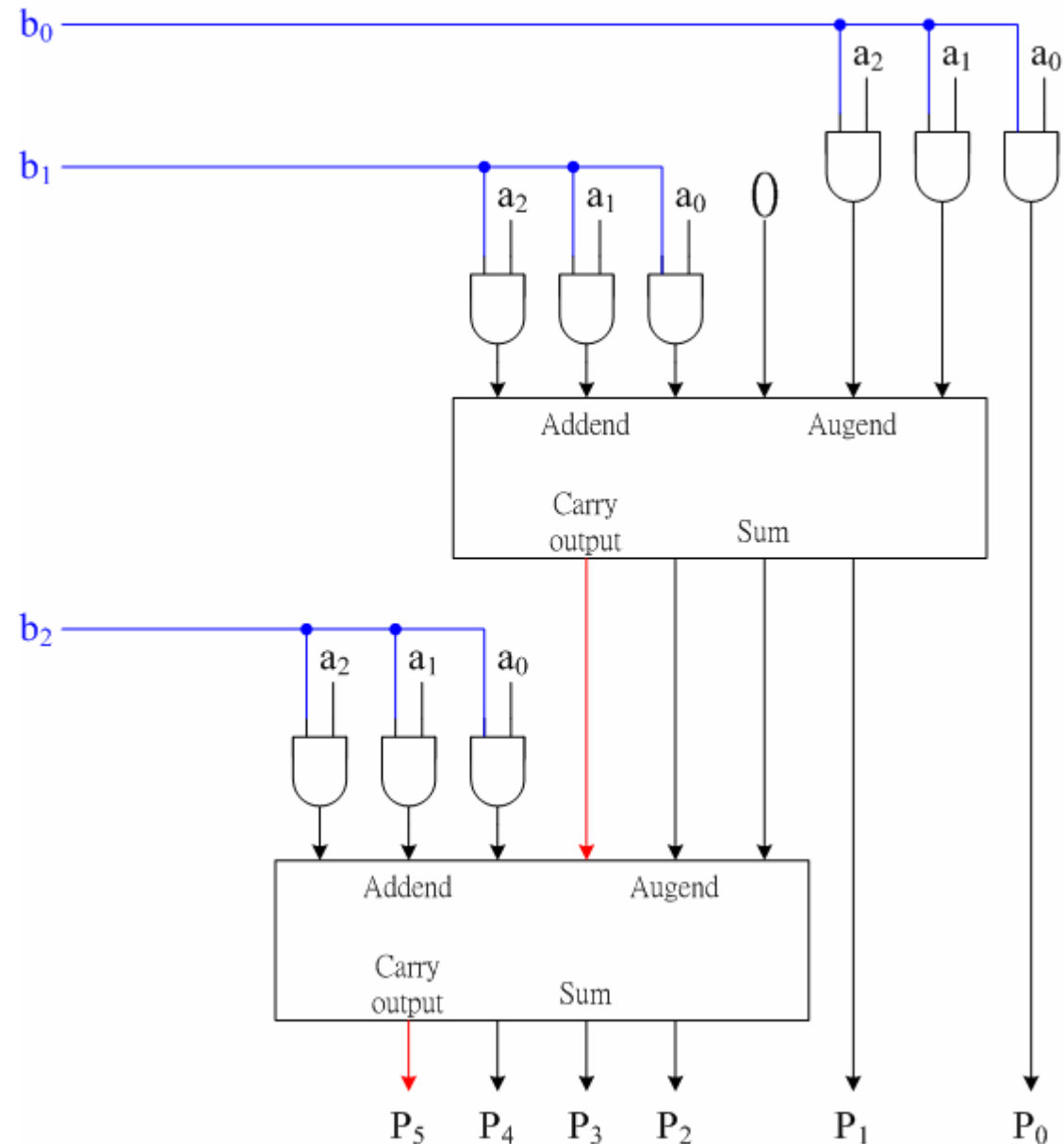5. Design a binary multiplier that multiplies two 3-bit unsigned numbers. Use AND gates and binary adders.

<Ans>

$$\begin{array}{r}
 \begin{array}{r}
 \text{X)} \\
 \hline
 \begin{array}{r}
 a_2 \quad a_1 \quad a_0 \\
 b_2 \quad b_1 \quad b_0 \\
 \hline
 a_2b_0 \quad a_1b_0 \quad a_0b_0 \\
 a_2b_1 \quad a_1b_1 \quad a_0b_1 \\
 +) \quad a_2b_2 \quad a_1b_2 \quad a_0b_2 \\
 \hline
 P_5 \quad P_4 \quad P_3 \quad P_2 \quad P_1 \quad P_0
 \end{array}
 \end{array}
 \end{array}$$



6. Design a circuit that multiplies a 4-bit multiplicand (被乗數) by the constant 1010 by applying contraction to the solution to Problem 5.

<Ans>

$$\begin{array}{r}
 \begin{array}{cccc}
 & a_3 & a_2 & a_1 & a_0 \\
 \times & 1 & 0 & 1 & 0 \\
 \hline
 & 0 & 0 & 0 & 0 \\
 a_3 & a_2 & a_1 & a_0 & \\
 0 & 0 & 0 & 0 & \\
 +) & a_3 & a_2 & a_1 & a_0 \\
 \hline
 P_7 & P_6 & P_5 & P_4 & P_3 & P_2 & P_1 & P_0
 \end{array}
 \end{array}$$

$$a_3 a_2 a_1 a_0 \times 1010 = P_7 P_6 P_5 P_4 P_3 P_2 P_1 P_0$$

$$P_0 = 0$$

$$P_1 = a_0$$

$$P_2 = a_1$$

$$P_3 = S(a_2 + a_0)$$

$$P_4 = S(C(P_3) + a_3 + a_1)$$

$$P_5 = S(C(P_4) + a_2)$$

$$P_6 = S(C(P_5) + a_3)$$

$$P_7 = C(P_6)$$

